

# Digital Systems Electronics Laboratory 02

Group 13

s295391 Giorgio Zoccatelli

s295567 Vittorio Macripò

Due Date: April 8, 2024  
Delivery date: March 10, 2024  
Instructor: Professor Guido Masera



**POLITECNICO  
DI TORINO**

Dipartimento di  
Elettronica e  
Telecomunicazioni



Politecnico di Torino  
Accademic Year 2023/24

# Contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>4-bit Sequential RCA</b>	<b>3</b>
2.1	Design entry . . . . .	3
2.2	Functional Simulation . . . . .	3
2.3	Synthesis . . . . .	4
<b>3</b>	<b>4-bit Sequential Adder/Subtractor</b>	<b>5</b>
3.1	Design entry . . . . .	5
3.2	Functional Simulation . . . . .	5
3.3	Synthesis . . . . .	5
<b>4</b>	<b>16-bit RCA, Carry-Bypass Adder and Carry-Select Adder</b>	<b>5</b>
4.1	Design entry . . . . .	5
4.2	Functional Simulation . . . . .	5
4.3	Synthesis . . . . .	5
<b>5</b>	<b>Multiplier</b>	<b>5</b>
5.1	Design entry . . . . .	5
5.2	Functional Simulation . . . . .	5
5.3	Synthesis . . . . .	5

# 1 Introduction

The purpose of this laboratory experience is to implement different circuits that can execute the basic operations of addition, subtraction and multiplication between binary numbers. We will also go through a more depth time analysis pointing out the different working frequencies of these circuits and finding out the critical paths for each case. Please notice that for the further descriptions, although we double checked that the overflow operation worked correctly on the singular testbenches, it seems to stop working when including the *.vho* and *.sdo* files in ModelSim.

## 2 4-bit Sequential RCA

### 2.1 Design entry

For the first exercise we want to describe a sequential 4-bit ripple-carry adder that supports signed numbers in 2's-complement: to do so we need the following designs:

- Three registers that will be updated every rising clock edge occurrence. Two of them will store the terms of the sum given by switches  $SW_{7-4}$  and  $SW_{3-0}$  and the third will store the result of the sum. This design is implemented in *regn.vhd*.
- A ripple-carry adder which is the heart of our circuit will take as an input the values to sum and will give as an output the result and the carry out (in this example we are not yet implementing the subtraction so the carry in will be always set to 0). To correctly sum two 4-bit signed numbers know from the theory that we can split the circuit in four connected full adders so for this purpose we will create two designs: *full\_adder.vhd* and *ripple\_adder.vhd*.
- After the sum operation we want to know if an overflow is occurring. We know from the theory that a 4-bit number in 2's-complement can correctly represent values from -8 to 7 and more precisely we can notice that the overflow occurs only when the carry out of the MSB is different from the MSB of the sum and at the same time the carry out must be different from the carry in of the LSB. This operation is described in *overflow\_check.vhd*.
- We want to visually see on the FPGA whenever an overflow is occurring so we store the result in a D-type Flip Flop that will trigger the  $LED_9$ . The Flip Flop is described in *flipflop.vhd*.
- We want to visually see on the FPGA the sum displayed following the hexadecimal systems so as we did for the previous laboratory activity we need a 7-segment decoder described in *display\_hexadecimal.vhd*.

All these designs are hierarchically described in a top entity *fourbit\_rca.vhd* where a unique clock signal driven by  $KEY_1$  and a unique reset signal  $KEY_0$  are assigned to all the memory elements.

### 2.2 Functional Simulation

In this section we want to implement a testbench to correctly simulate the behavior of our circuit. The rules to apply the testbench signals are well known but we want to point out how to correctly implement the clock and reset signals:

- $KEY_0$  and  $KEY_1$  are initially set to 0 which means by convention that the reset signal is high and the clock signal is down.
- After giving a starting input configuration to the switches we set  $KEY_0$  to 1 (reset low) and  $KEY_1$  to 1 (clock high) so that the two registers of the sum will change their output following the switches configuration and the ripple-carry adder can properly sum the two values. This combinational circuit will then give the result of the sum and the carry out to the third register and to the Flip Flop after the overflow is checked.
- Without changing the state of  $KEY_0$  we set  $KEY_1$  to 0 and then again to 1 so that at the second rising edge of the clock we can change the output of the third register as well as the output of the Flip Flop triggering both the HEX displays and the LEDR<sub>9</sub>.
- We can finish a test cycle by setting both  $KEY_1$  and  $KEY_0$ .

## 2.3 Synthesis

With the synthesis we want to test the correct functioning of our circuit and we want to analyse the time constraints regarding the clock period and the worst case delay through memory elements.

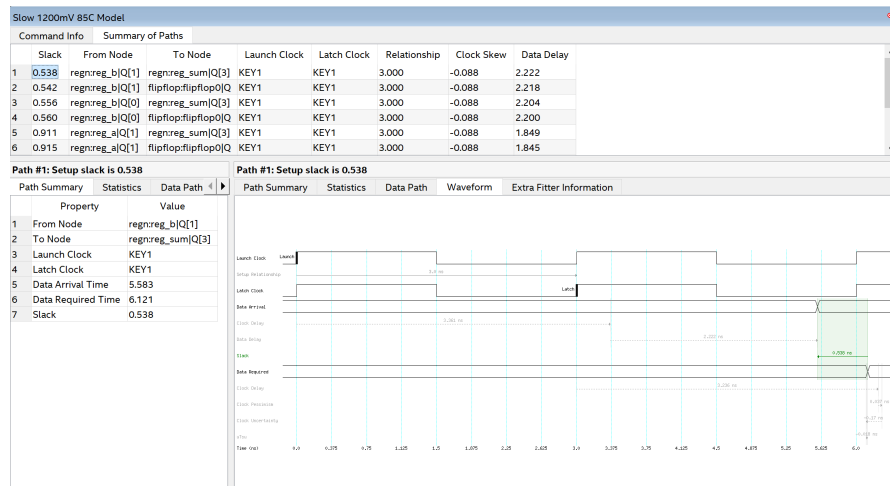


Figure 1: Circuit delays

In Figure 1 we can see that using a clock signal with a period of 3 ns we obtain a circuit with a maximum operating frequency  $f_{\max}$  equal to 406.17 Hz. The same figure also points out that our longest path through the circuit in terms of delay is the one going from *reg\_b* (one of the two registers for the sum terms) to *reg\_sum* (the register storing the result of the sum). By importing our testbench on ModelSim as well as the *.vho* and *.sdo* files we can then analyse the testbench with respect to all the internal signals delays.

In Figure 2 we can see an overall timing evolution of the circuit while in Figure 3 we can see as a proof of the correct delay representation the transition between the reset and the display of the sum terms -3 and -4 occurring in the second testbench configuration.

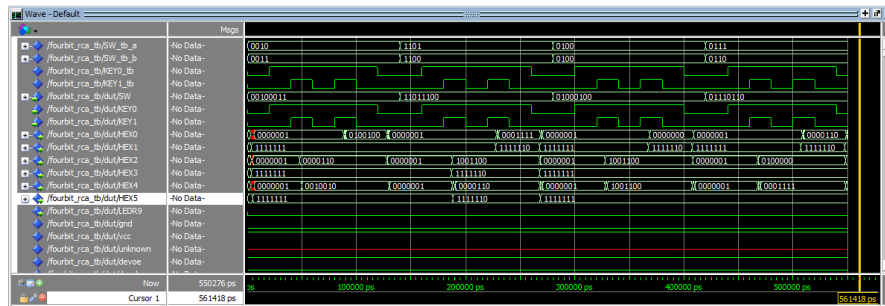


Figure 2: Overall testbench

 


Figure 3: Particular delayed transition

### 3 4-bit Sequential Adder/Subtractor

#### 3.1 Design entry

#### 3.2 Functional Simulation

#### 3.3 Synthesis

### 4 16-bit RCA, Carry-Bypass Adder and Carry-Select Adder

#### 4.1 Design entry

#### 4.2 Functional Simulation

#### 4.3 Synthesis

### 5 Multiplier

#### 5.1 Design entry

#### 5.2 Functional Simulation

#### 5.3 Synthesis